

第三章作业

提交方式请按照文件“2026 电路与数字逻辑作业、课堂练习提交说明.pdf”的要求

请于2026年4月9日（周四23:59PM）前提交。

问题包括：


(1) 教材第108页： 3.2, 3.3, 3.4

(2) T1, T2, T3, T4

T1: Draw the diagrams of three ways to deal with unused inputs of CMOS circuit.

T2: What are the three states of the three-state buffer?

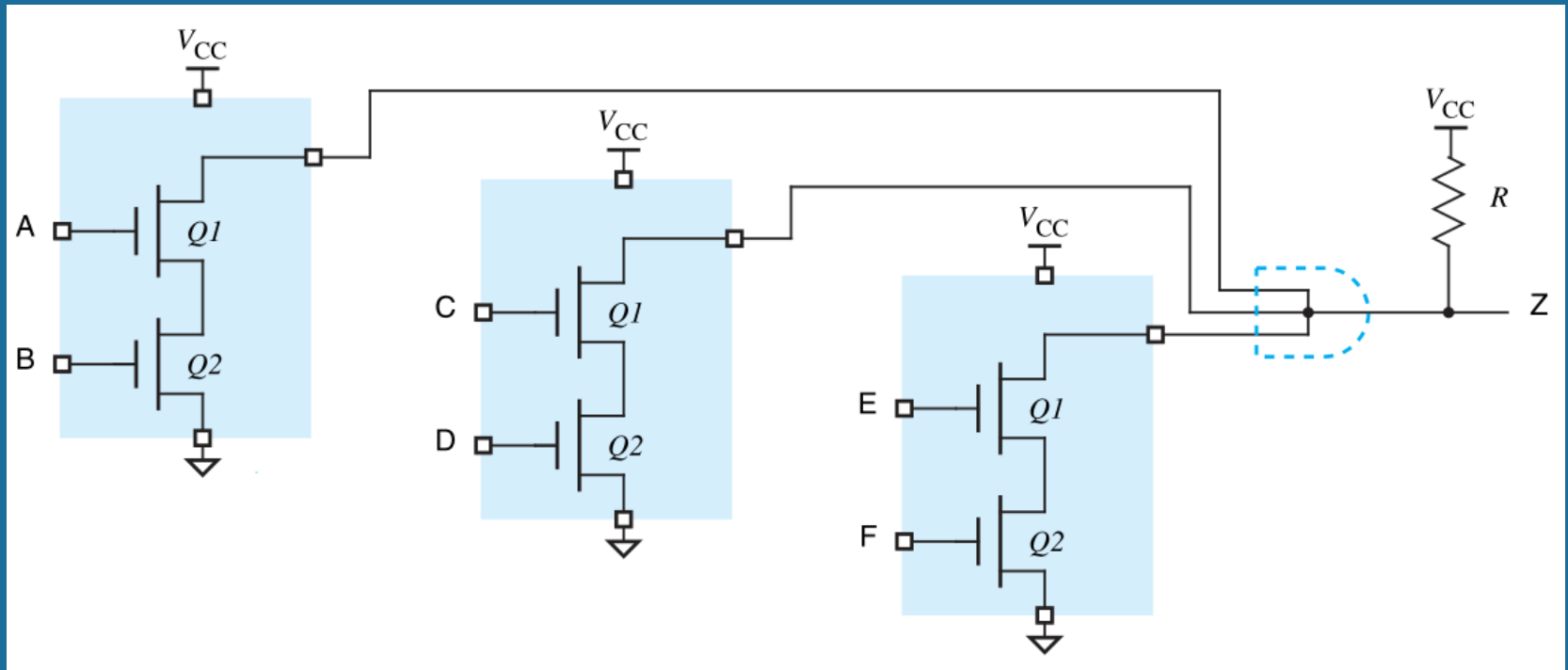T3: Write the logic function of Z in the following figure. What is the name for the circuit connection in the blue dotted line area of the figure?



T4: Determine the Thevenin and Norton equivalents for left side of port a-b of the circuit below.

$$V = 6 \text{ V}; I = 2 \text{ A}; R_1 = 6 \Omega; R_2 = 3 \Omega; R_3 = 2 \Omega$$

