
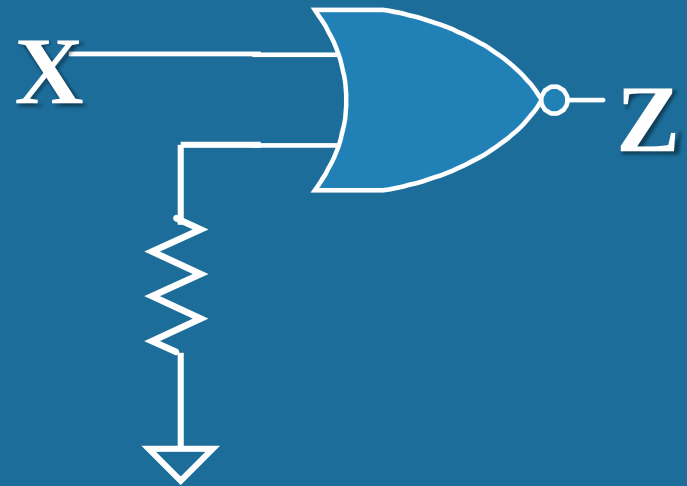
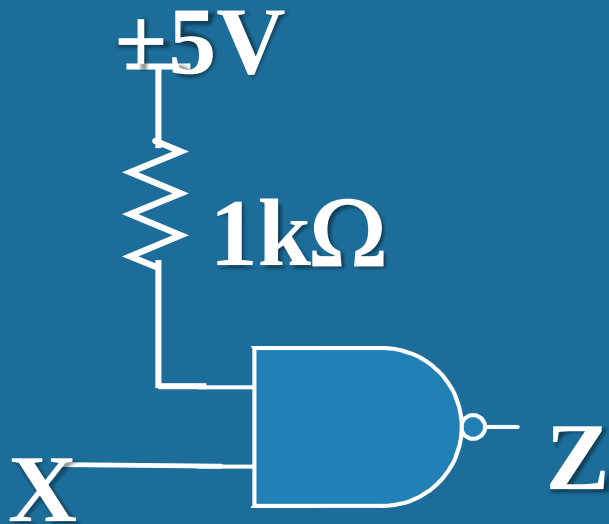


第三章作业 答案

T1: Draw the diagrams of three ways to deal with unused inputs of CMOS circuit.

T1: Unused inputs of CMOS circuit

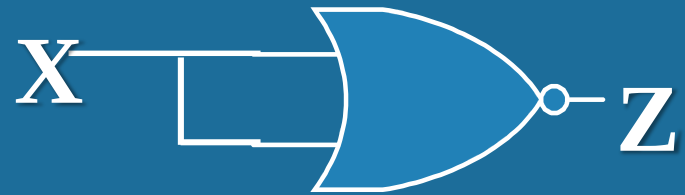

T2: What are the three states of the three-state buffer?


T2: Three-state Buffer

$EN=0$,

$C=1$, T_p is OFF

$B=1$, $D=0$, T_n is OFF

OUT is floating state

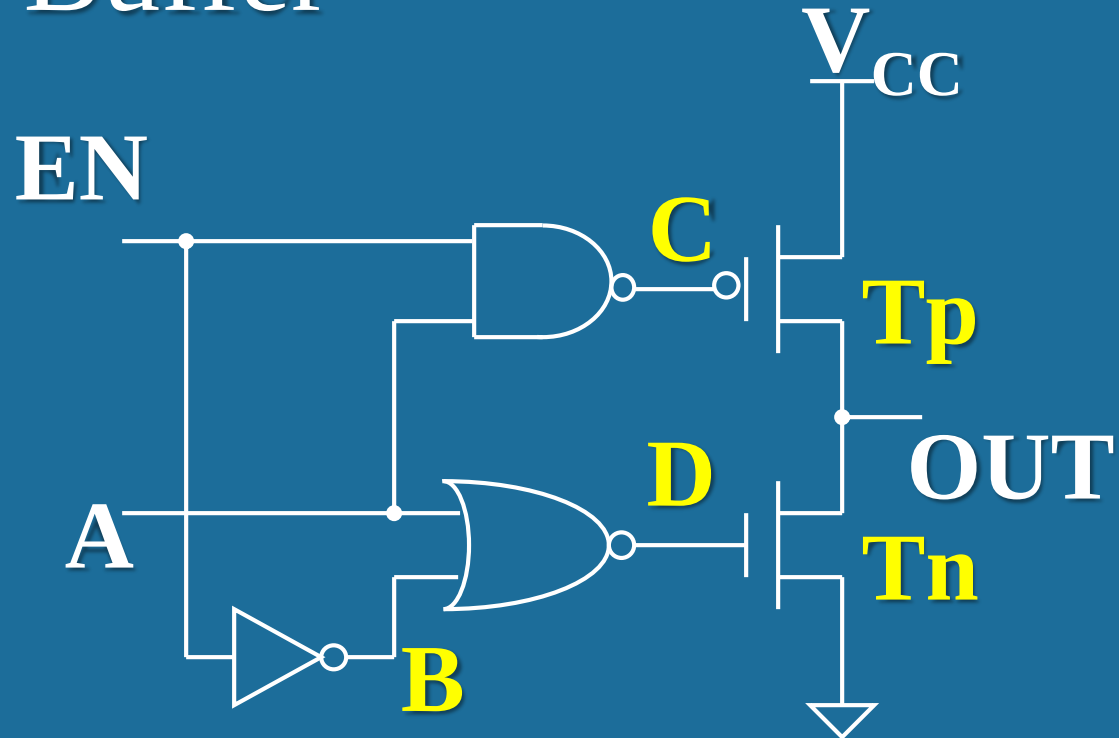

$EN=1$,


$C=\bar{A}$, $B=0$, $D=\bar{A}$

OUT=A



OUT is low-state or high-state

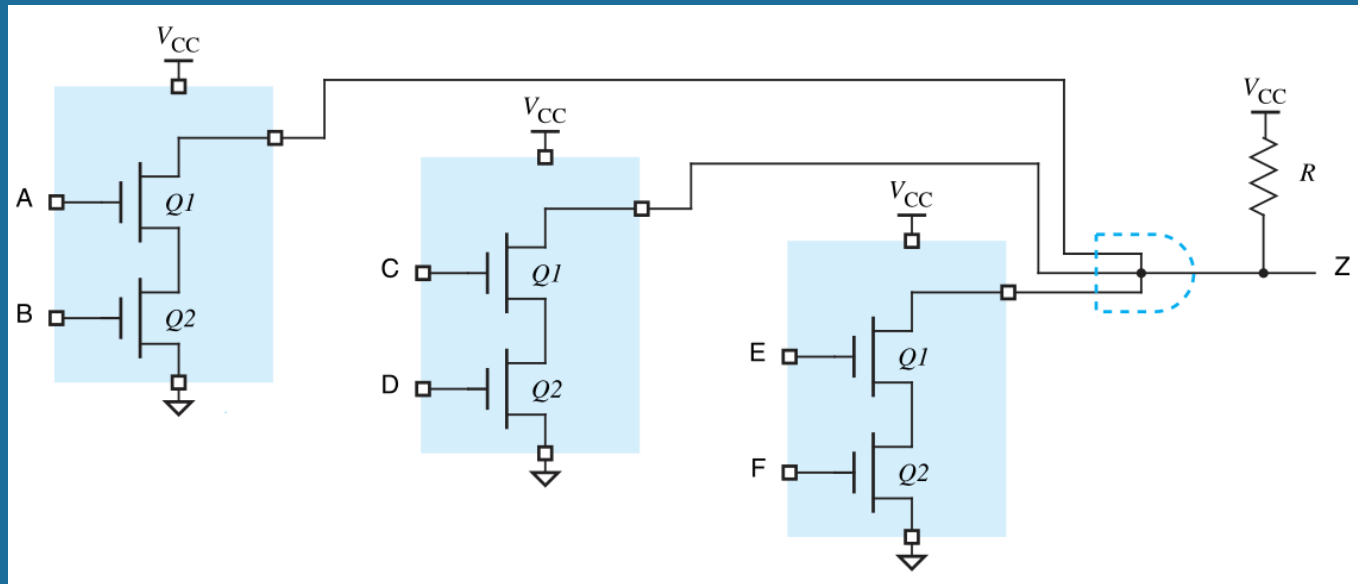T3: Write the logic function of Z in the following figure. What is the name for the circuit connection in the blue dotted line area of the figure?




$$Z = \overline{AB + CD + EF}$$

Name: "Wired AND"



T4: Determine the Thevenin and Norton equivalents for left side of port a-b of the circuit below.
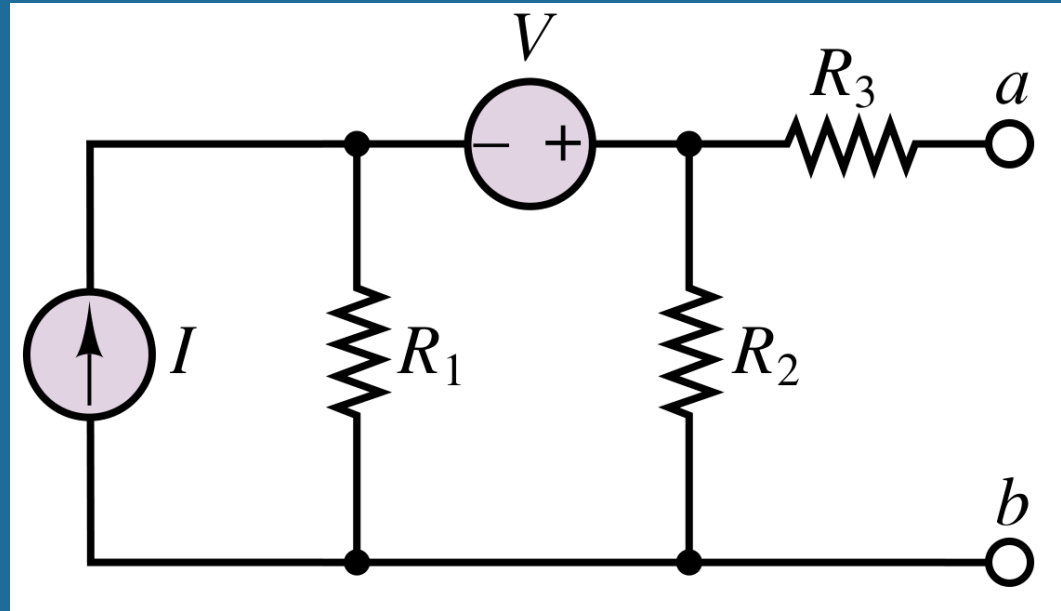
$$V = 6 \text{ V}; I = 2 \text{ A}; R_1 = 6\Omega; R_2 = 3\Omega; R_3 = 2\Omega$$



$$V_{ab} = V_I + V_v = 2A \times \frac{3\Omega \times 6\Omega}{3\Omega + 6\Omega} + V \times \frac{3\Omega}{3\Omega + 6\Omega} = 4V + 2V = 6V$$
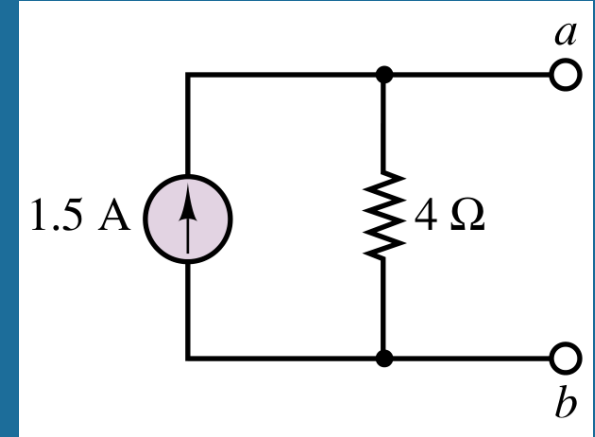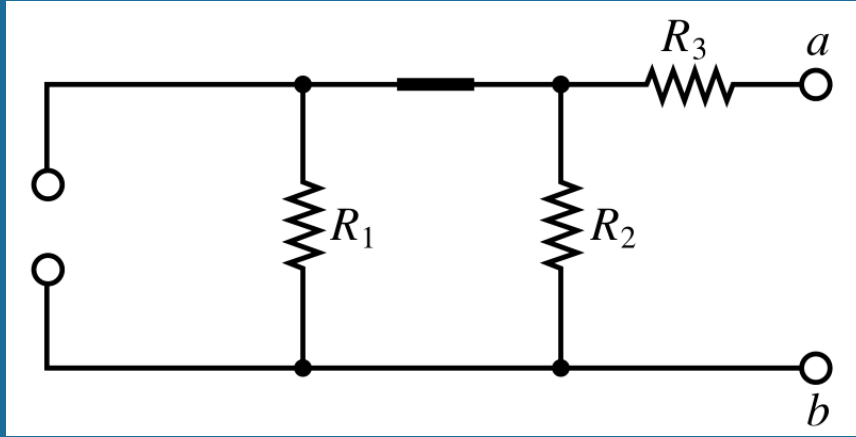
$$R_T = R_1 \parallel R_2 + R_3 = 6 \parallel 3 + 2 = 4\Omega$$



$$R_T = R_1 \parallel R_2 + R_3 = 6 \parallel 3 + 2 = 4\ \Omega$$

$$V_{ab} = V_I + V_v = 2\text{ A} \times \frac{3\ \Omega \times 6\ \Omega}{3\ \Omega + 6\ \Omega} + V \times \frac{3\ \Omega}{3\ \Omega + 6\ \Omega} = 4\text{ V} + 2\text{ V} = 6\text{ V}$$

$$R_T = R_N = R_{eq}$$

$$I_N = \frac{V_{ab}}{R_T} = \frac{6\text{ V}}{4\ \Omega} = 1.5\text{ A}$$